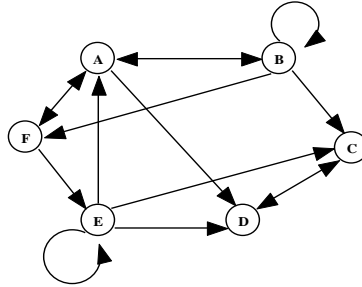


JUNIOR DIVISION

1. Graph Theory


Draw the adjacency matrix for the directed graph at the right?



1.

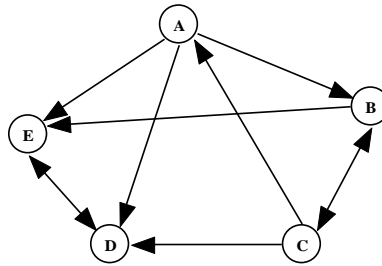2. Graph Theory


How many paths of length 2 are there in the directed graph at the right?



2.

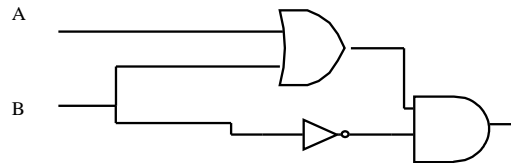3. Digital Electronics


Which ordered pairs make the digital circuit at the right TRUE?



3.

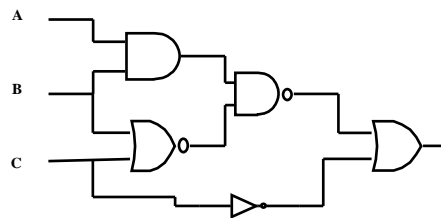4. Digital Electronics

Translate the digital circuit at the right to its equivalent Boolean expression. Do not simplify.



4.

JUNIOR DIVISION**5. What Does This Program Do? - Strings**

What is the output when this program is run?

```
A="NEWJERSEYISTHEGARDENSTATE"
B=""; C=""; D=""; E=""; F=""
for x = 0 to len(A) - 1
    if A[x:x] < "K" then
        B = B + A[x:x]
    else
        C = C + A[x:x]
    end if
next x
for x = 0 to len(B) - 1
    if B[x:x] != "E" then
        D = D + B[x:x]
    end if
    if C[x:x] != "S" then
        E = E + C[x:x]
    end if
next x
for x = 0 to 5
    if ((D[x:x] != "A") && (E[x:x] != "R")) then
        F = D[x:x] + F + E[x:x]
    end if
next x
output F
end
```

5.